
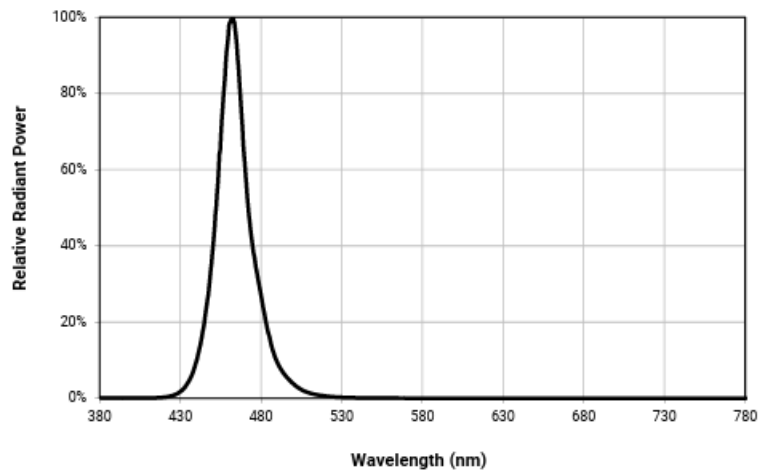


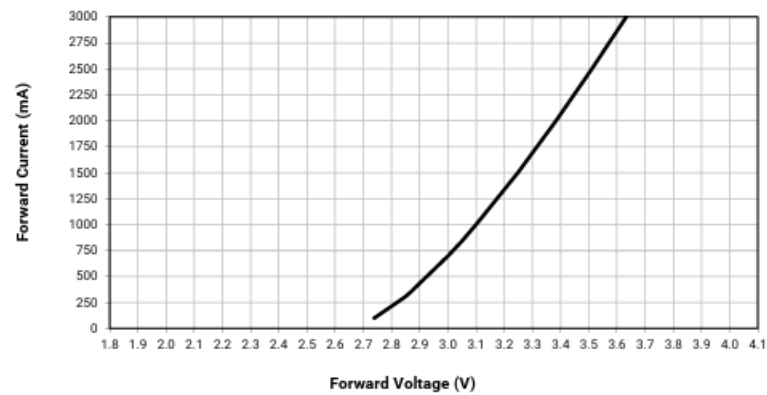
ELECTRICAL CHARACTERISTICS - BLUE (T_J = 25 °C)



RELATIVE SPECTRAL POWER DISTRIBUTION - BLUE



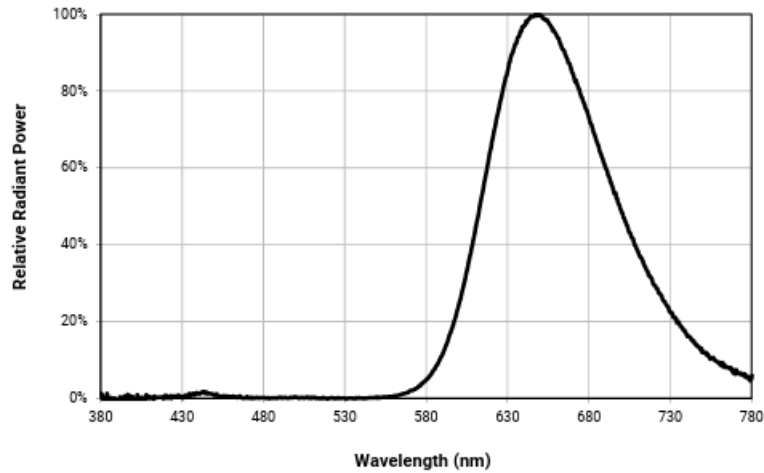ELECTRICAL CHARACTERISTICS - PC RED (T_J = 25 °C)



RELATIVE SPECTRAL POWER DISTRIBUTION - PC RED

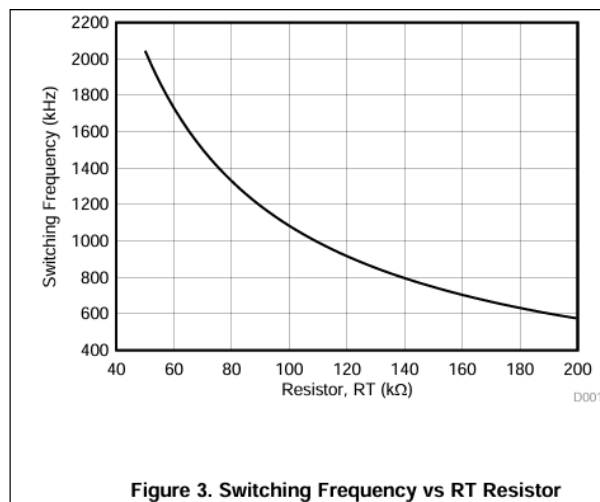


Figure 3. Switching Frequency vs R_T Resistor



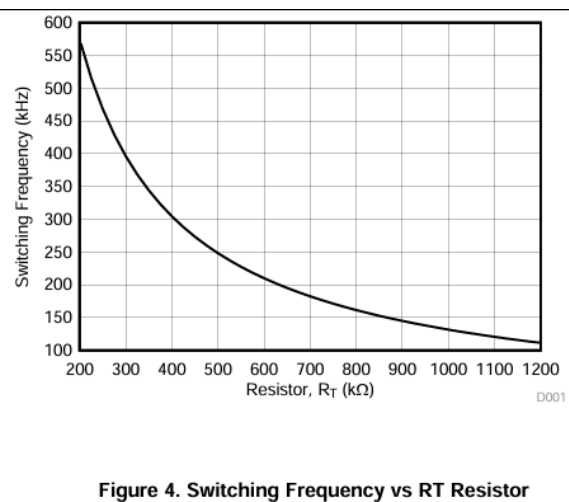


Figure 4. Switching Frequency vs R_T Resistor

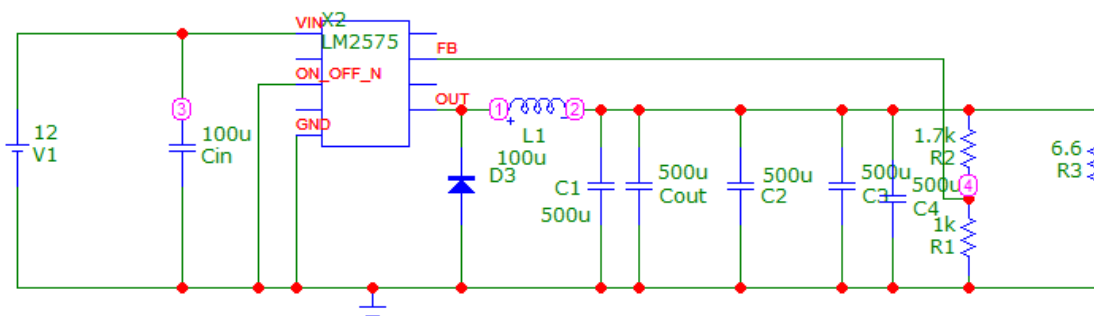
The value for the R_T Resistor required to set the switching frequency of the TPS92512




3.3V Buck Converter

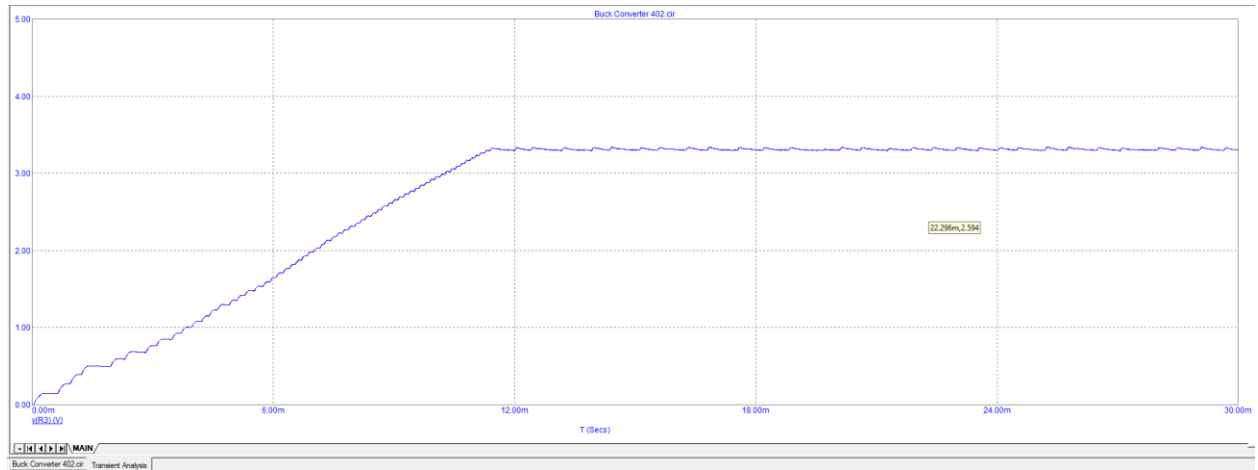


Transient at the Load

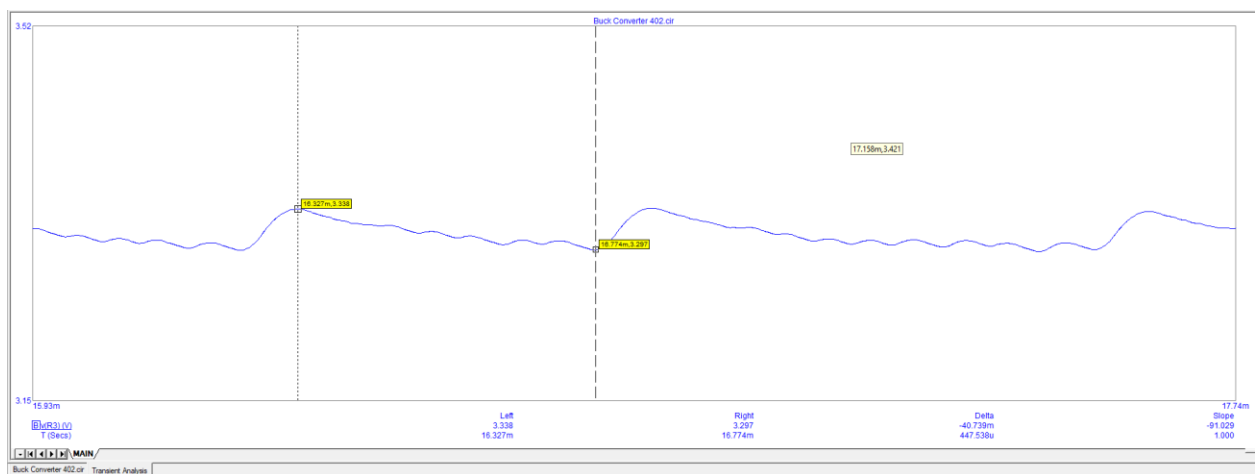


p-p Ripple

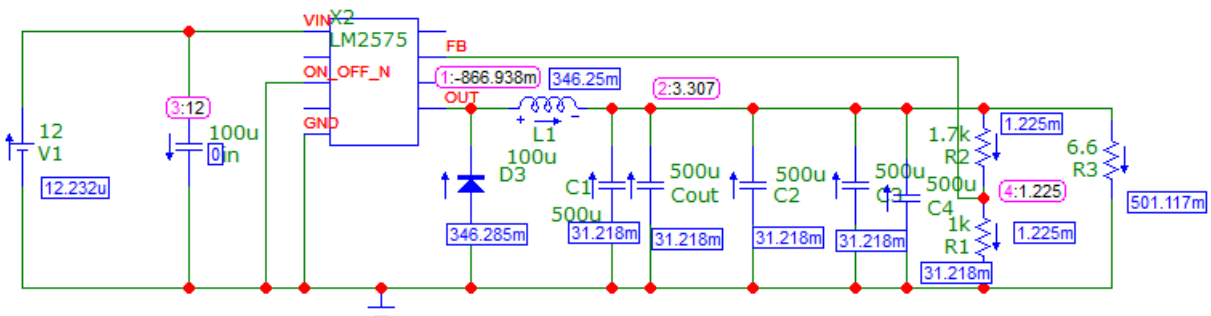


Node Voltages and Current

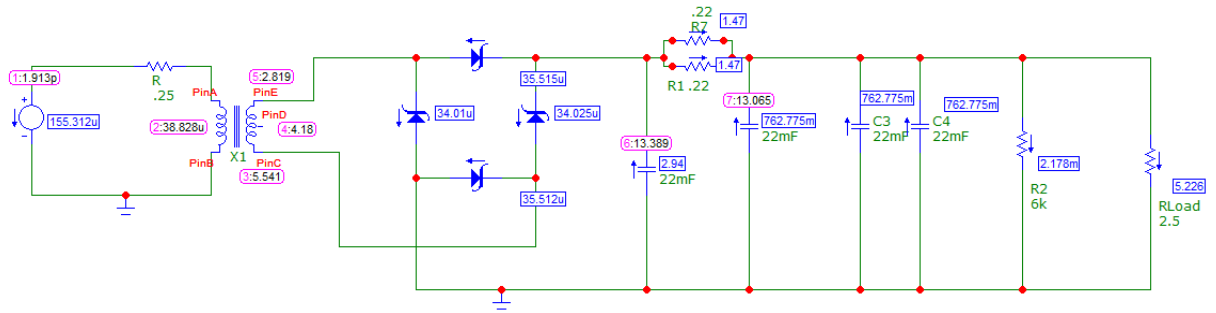


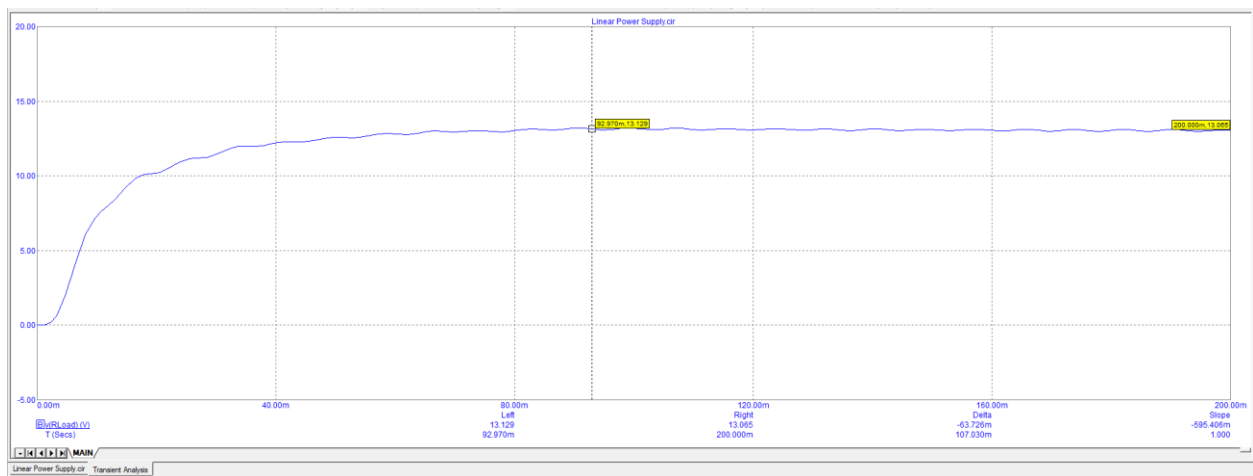Linear Power Supply Node Voltages and Current




Linear Power Supply Transient

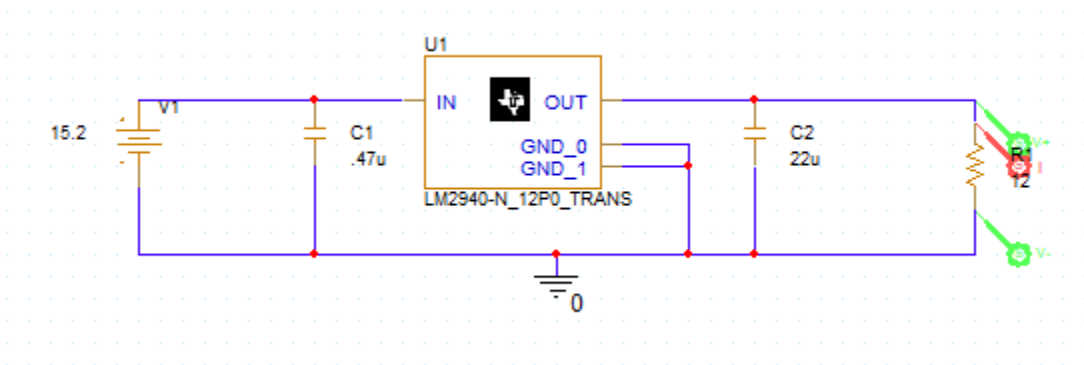


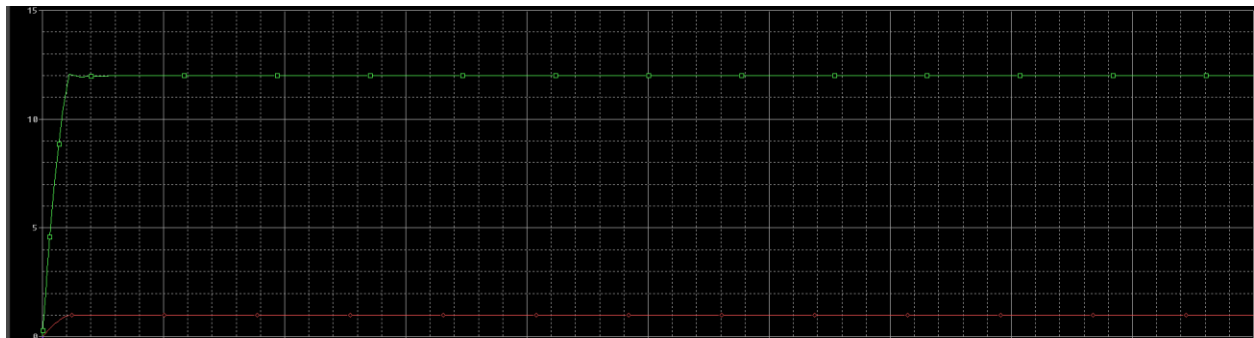


12V Regulator Transient Response

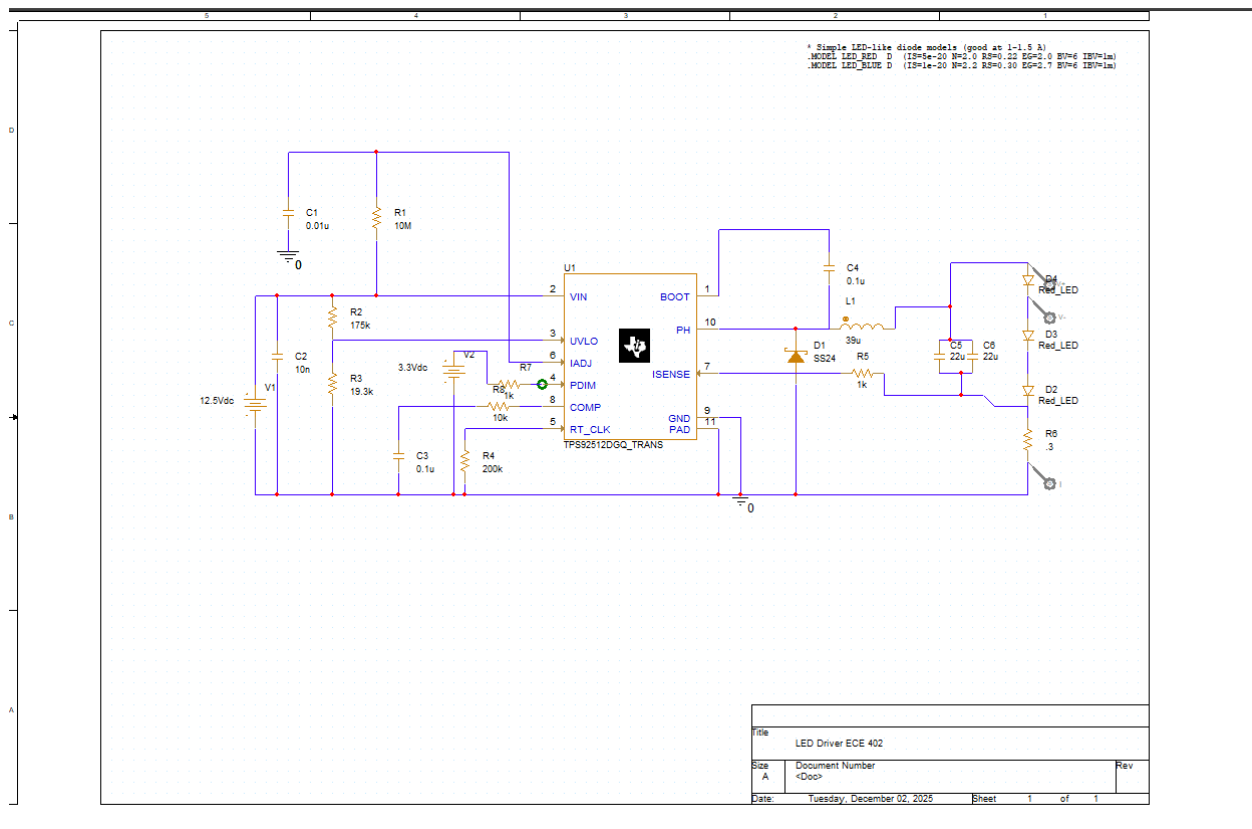


LED Driver Sim

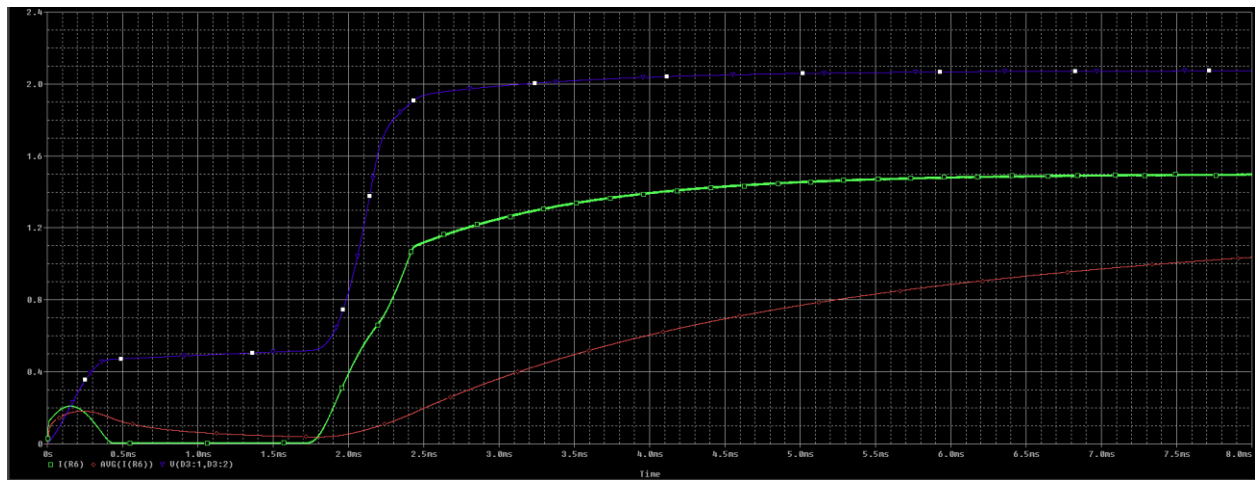

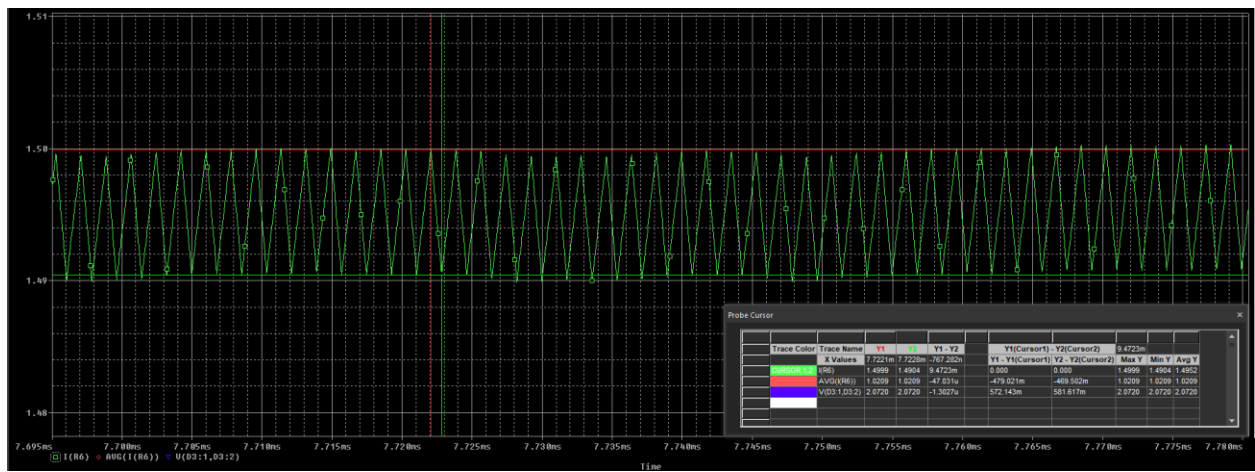Blue \rightarrow V_f of Led, Green \rightarrow $I(R6)$



Current Ripple through Risense

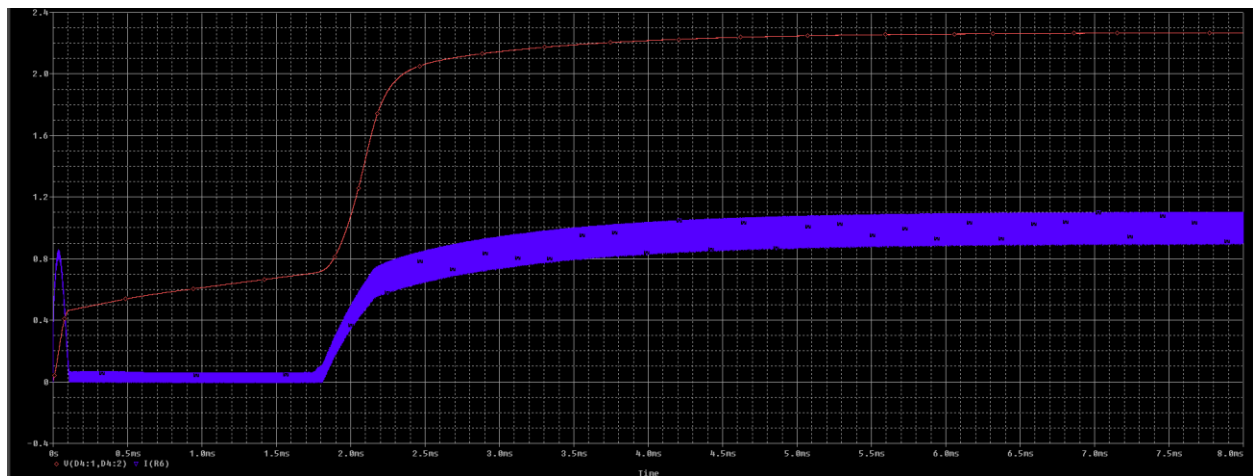

LED Driver Sim with 15.2V V_{in} , and 33 μ H Inductor -> Increased Current Ripple Through isense resistor, still low inductor ripple tho. Red-> V_f of LED, Blue->Current through R6.